

The background of the slide is a light gray with a fine grid pattern. It is decorated with various mechanical illustrations. In the top left, there are yellow and green gears with a green shaft. In the top center, a large green gear is connected to a smaller yellow gear. In the top right, a green gear is connected to a red shaft. In the middle right, there is a complex arrangement of yellow and green gears, some with internal patterns, and a black and yellow striped band. In the bottom left, a green gear is connected to a yellow gear. In the bottom center, a green gear is connected to a red shaft. In the bottom right, a green gear is connected to a red shaft.

Automatic Street Light /Dark Detector Circuit

ECE3570 Project

Presented by: Abid Ahmad


Date: 3/31/26



What the Project Is About

This project is an automatic street light circuit that uses an LDR sensor and an op-amp to detect light intensity. The circuit turns the LED on when it becomes dark and turns it off when there is enough light.

Main idea:

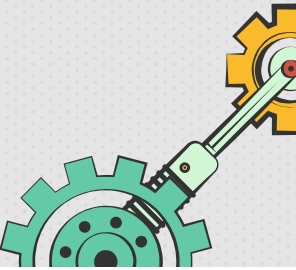- Detect surrounding light level automatically
 - Compare the sensor voltage with a reference voltage
 - Control the LED output based on light conditions
- 



Purpose and Real-World Application

Purpose

- To design a circuit that automatically responds to changes in light conditions
 - To reduce manual switching of lights
- To demonstrate how sensors and op-amps can be used in control systems

Real-World Application

- automatic street lighting
- garden and outdoor lights
- security lighting systems
 - parking lot lighting
- energy-saving smart lighting systems


Components and Circuit Description


Components Used

- LM741 Op-Amp
- LDR (Light Dependent Resistor)
 - 10k Ω Resistor
 - Potentiometer
 - 220 Ω Resistor
 - LED
 - 9V Battery
- Breadboard and jumper wires

Circuit Description

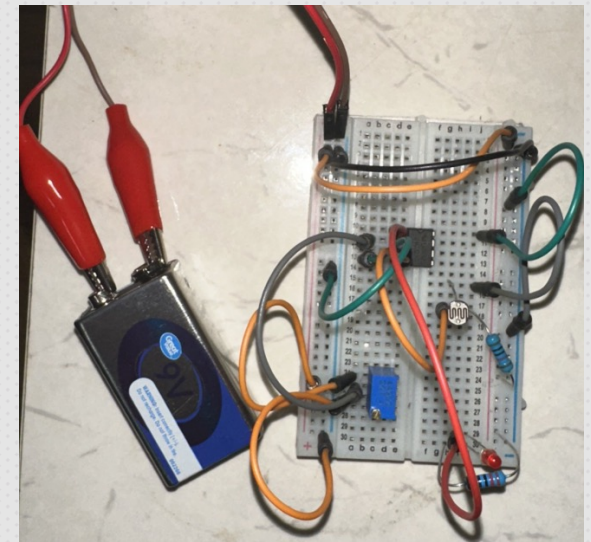- The LDR and 10k Ω resistor form a voltage divider
 - The potentiometer sets the reference voltage
- The op-amp compares the LDR voltage with the reference voltage
 - The LED turns ON or OFF depending on the light level



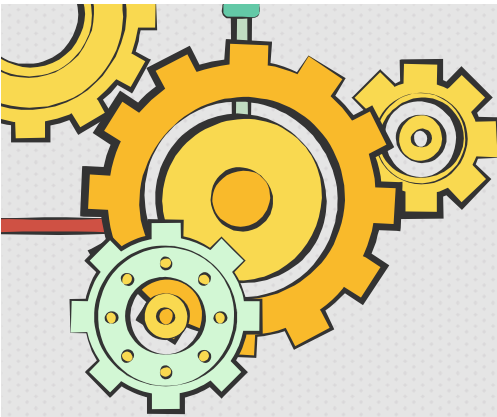

Benefits, Drawbacks, and Real-Life Implementation


Benefits


- simple and low-cost design
 - automatic operation
 - saves energy
 - easy to build and understand
- useful for basic smart-lighting applications

Drawbacks

- sensitivity needs adjustment using the potentiometer
- performance can change with surrounding light conditions
- the LM741 is not the best op-amp for single-supply operation
- the circuit is suitable for small loads unless extra components are added

Real-Life Implementation

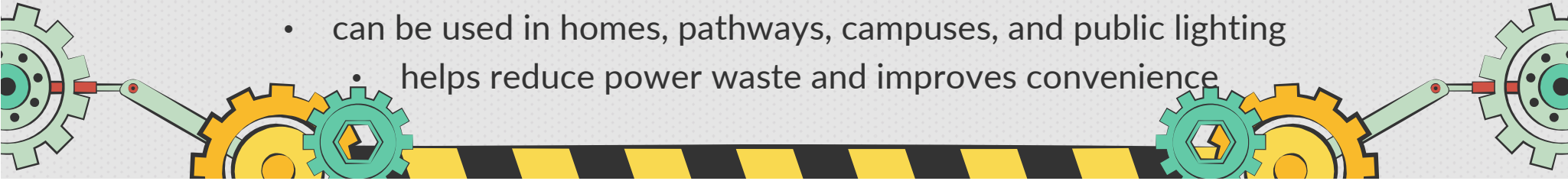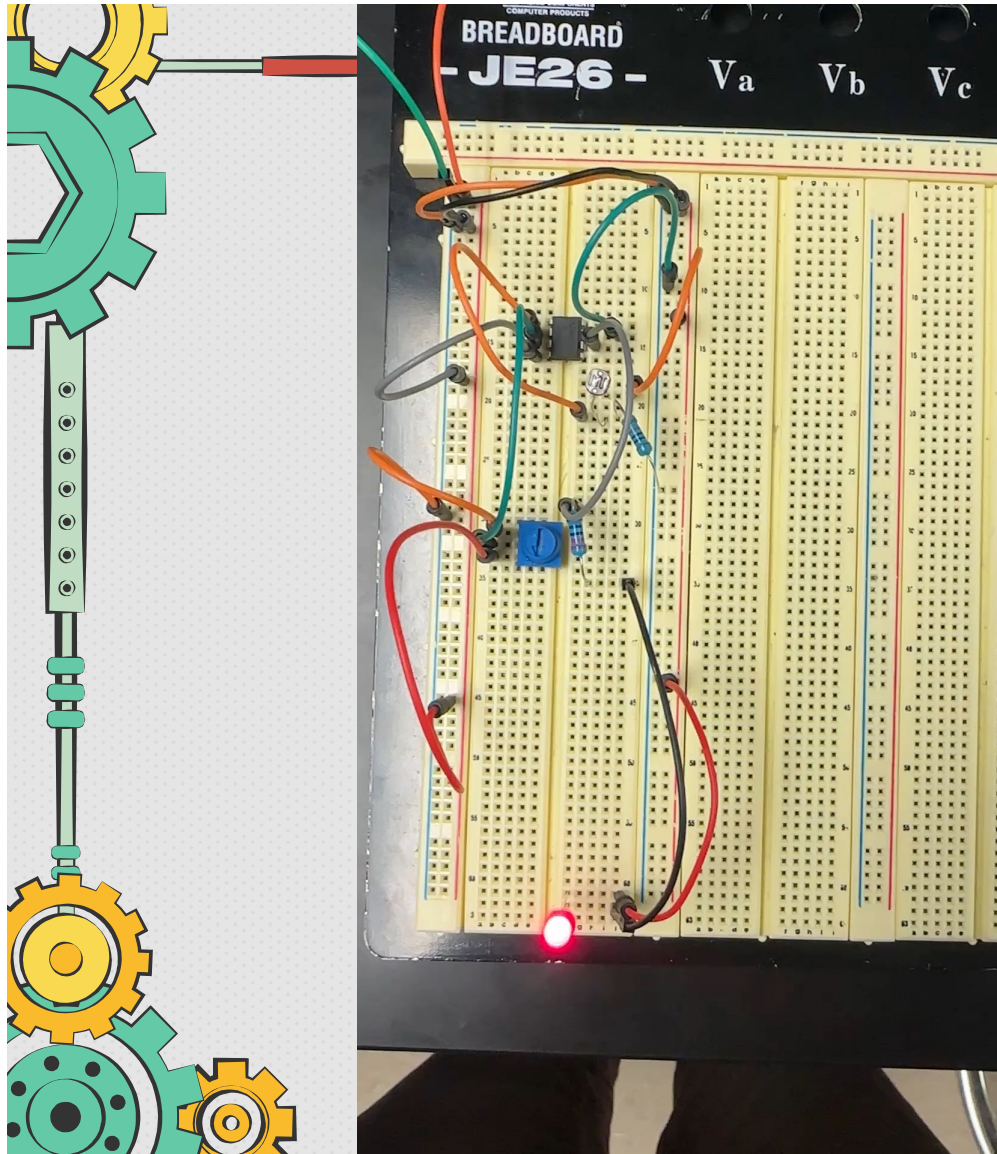- can be connected to a transistor or relay to control larger lamps
 - can be used in homes, pathways, campuses, and public lighting
 - helps reduce power waste and improves convenience
- 



Project Demonstration Video



This LDR sensor detects light intensity in the project and helps the circuit turn the LED on in darkness and off in bright light.

This video shows:

- how the circuit responds to light and darkness
- LED turning on in dark conditions
- LED turning off in bright conditions
- the effect of adjusting the potentiometer
- the working model in real time